



Department of Electrical and Computer Engineering,
Gina Cody School of Engineering and Computer Science,
Concordia University, Montreal, Canada

COEN 6501: Digital Design and Synthesis

Design of an Arithmetic Unit Performing $Z = 1/4 [A * B] + 1$

Abishek Arumugam Thiruselvi - 40218896

Manish Pejathaya - 40194909


Mahsa Vahed - 40183415

November 2022

Abstract

The objective of this project is to create an arithmetic device that can compute $Z = 1/4 [A * B] + 1$. Two 16-bit unsigned operands, A and B, will be provided to the unit. When $LOAD = 1$, the data is latched by two clock-synchronous internal registers (RA and RB). The device produces results in a 32-bit format. END_FLAG is set high when the output is produced. In response to an asynchronous $CLEAR$ signal, all registers are set to 0. Array multiplier is selected for the multiplication operation.

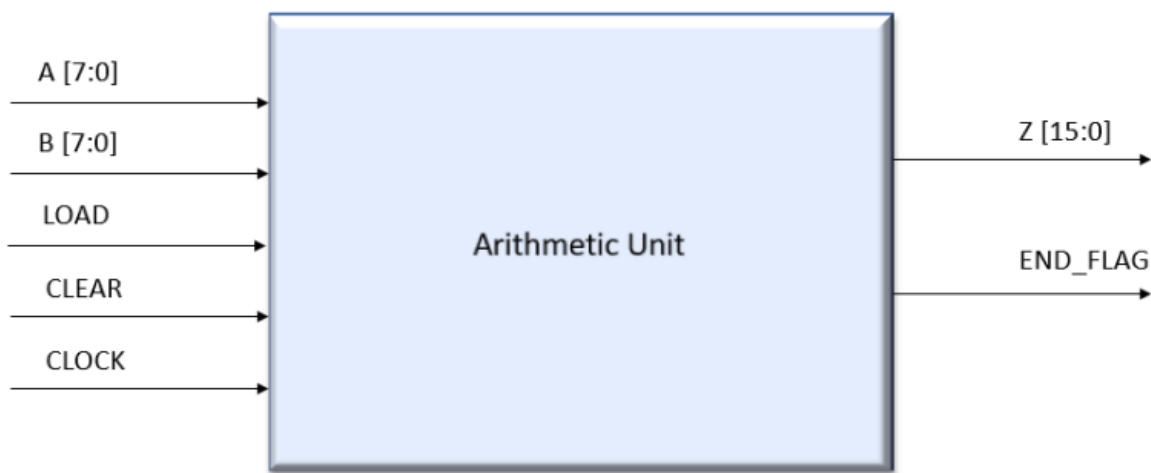Expansion of the method for 16 bits operands and Pipelining of the design are the Extra features for our project.



Contents

Abstract.....	2
Introduction	5
Signal Specifications.....	5
Proposed Algorithm in Pipeline	6
Data Path Stages are described as follows:	6
DESIGN AND ANALYSIS OF COMPONENTS	6
NOT	6
AND.....	7
Mux2:1	7
D-Flip Flop	8
Full Adder	9
RTL synthesis and Testing of various built combinational components.....	9
DFF	10
MUX	11
FULL ADDER	12
Multiplier	14
Multiplier Design.....	15
Design of an 8-bit Multiplier	15
Design of a 16-bit multiplier using 8-bit multiplier	17
Technical implementation	18
Implementation of CLEAR operation	18
Implementation of LOAD operation	18
Implementation of the END FLAG.....	18
Implementation of the Arithmetic Unit.....	18
Experiment Result.....	20
Precision RTL Area Report.....	22
RESOURCES	23
CHALLENGES	23
CONCLUSION.....	23
References	24

Table of Figures

Figure 1: NOT Gate.....	6
Figure 2: AND Gate	7
Figure 3: MUX2:1 Gate.....	7
Figure 4: Mux Detailed Gate	7
Figure 5: DFF Gate.....	8
Figure 6: DFF Detailed Gate	8
Figure 7: Full Adder.....	9
Figure 8: Full Adder Truth Table	9
Figure 9: DFF16 Synthesis	10
Figure 10: Simulation Result for DFF16.....	10
Figure 11: MUX Synthesis	11
Figure 12: Simulation Result for MUX.....	11
Figure 13: Full Adder Synthesis.....	12
Figure 14: Full Adder32 Synthesis.....	13
Figure 15: Simulation Result for Full Adder32	14
Figure 16: MULTIPLIER 16X16 Synthesis.....	14
Figure 17: Simulation Result for MULTIPLIER 16X16	15
Figure 18: Partial Product Design.....	16
Figure 19: 8-bit Array Multiplier Synthesis	16
Figure 20: Design of a 16-bit multiplier using 8-bit multiplier.....	17
Figure 21: Simulation Result Of TOP-Level	20
Figure 22: TOP-Level Synthesis	21
Figure 23: Device Utilization	22

Introduction

In arithmetic logic, multiplication is an important operation. The arithmetic-logic unit, a section of a central processing unit, carries logic and arithmetic functions on the operands of computer instruction.

The purpose of this project is to design an arithmetic unit capable of calculating $Z = 1/4 [A \times B] + 1$. This unit receives two unsigned 16-bit operands A and B. Two clock synchronous internal registers RA and RB latch the data when $LOAD = 1$. The unit outputs the results in a 16-bit register RZ output port, and END_F rises. An asynchronous CLEAR signal will clear all the registers to '0'. Expansion of the method for 32 bits operands and Pipelining of the design are added to the project as extra features. The product of $(A \times B)$ is computed and stored using flip flop if the control flag is high in stage 1, The division by 4 of the stage 1 result is computed and stored using flip flop if the control flag is high in stage 2, and the result of stage 2 is incremented by one and sent to mux to get the result Z in stage 3.

Signal Specifications

- A: Unsigned 16-bit Operand A
- B: Unsigned 16-bit Operand B
- Z: Signed Output
- CLEAR: Clears selected registers
- LOAD: Loads Operand into internal registers
- CLOCK: Input Clock
- END_F : Indicates end of operation

Proposed Algorithm in Pipeline

Data Path Stages are described as follows:


- Stage 1: The product of $A \times B$ is computed and stored using flip flop if the control flag is high
- Stage 2: The division by 4 of the stage 1 result is computed and stored using a flip flop if the control flag is high.
- Stage 3: The result of stage 2 is incremented by one and sent to mux to get the final result Z.

DESIGN AND ANALYSIS OF COMPONENTS

We use the basic logic gates. the following illustrations and tables show the circuit symbol and logic combinations of logic gates.

NOT

 The NOT gate, also known as an inverter, is a logic gate used in digital logic to implement logical negation. In mathematical logic, it is comparable to the logical negation operator. [1]



Truth Table

A	OUT
0	1
1	0

Figure 1: NOT Gate

AND

An AND gate is a logic gate. And it has two or more inputs and a single output. An AND gate operates on logical multiplications. In this gate, if one of the inputs is low or 0, then the output is also 0. If all the inputs are high or 1, then the output will be 1 or high. [1]

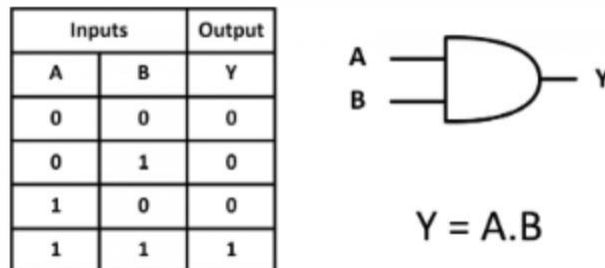


Figure 2:AND Gate

Mux2:1

Multiplexer is a combinational circuit that have many inputs and single output. Output is based on the control or select inputs. [1]

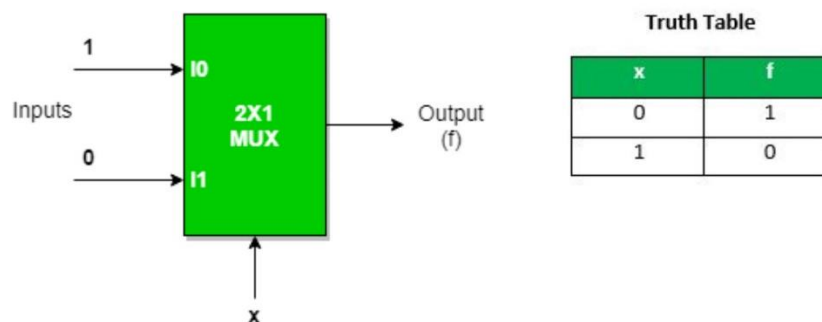


Figure 3: MUX2:1 Gate

 


Figure 4: Mux Detailed Gate

D-Flip Flop

A latch, often known as a flip-flop, is a circuit with two stable states that can be used to store state data. Signals which is applied to one or more inputs and one or two outputs allow the circuit to altering state. It guarantees that both inputs, S and R, are never equal to one at the same time. One of the key uses of a D flip flop is to add delay to a timing circuit so that data can be sampled at predetermined intervals.[1]

 


Figure 5: DFF Gate

 


Figure 6: DFF Detailed Gate

Full Adder

Full Adder is an adder that adds three inputs and generates two outputs. The inputs are A and B and carry as C-in. The output carry is C-out and the normal S, which is SUM. [2]

 


Figure 7: Full Adder

Inputs			Outputs	
A	B	C – IN	Sum	C - Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Figure 8: Full Adder Truth Table

RTL synthesis and Testing of various built combinational components

All RTL syntheses are compiled and synthesized by Mentor Graphics Precision RTL Synthesis. we described all gates we have used in our project with their functionality in above parts. In this part we will display all synthesis files.

DFF

 


Figure 9: DFF16 Synthesis

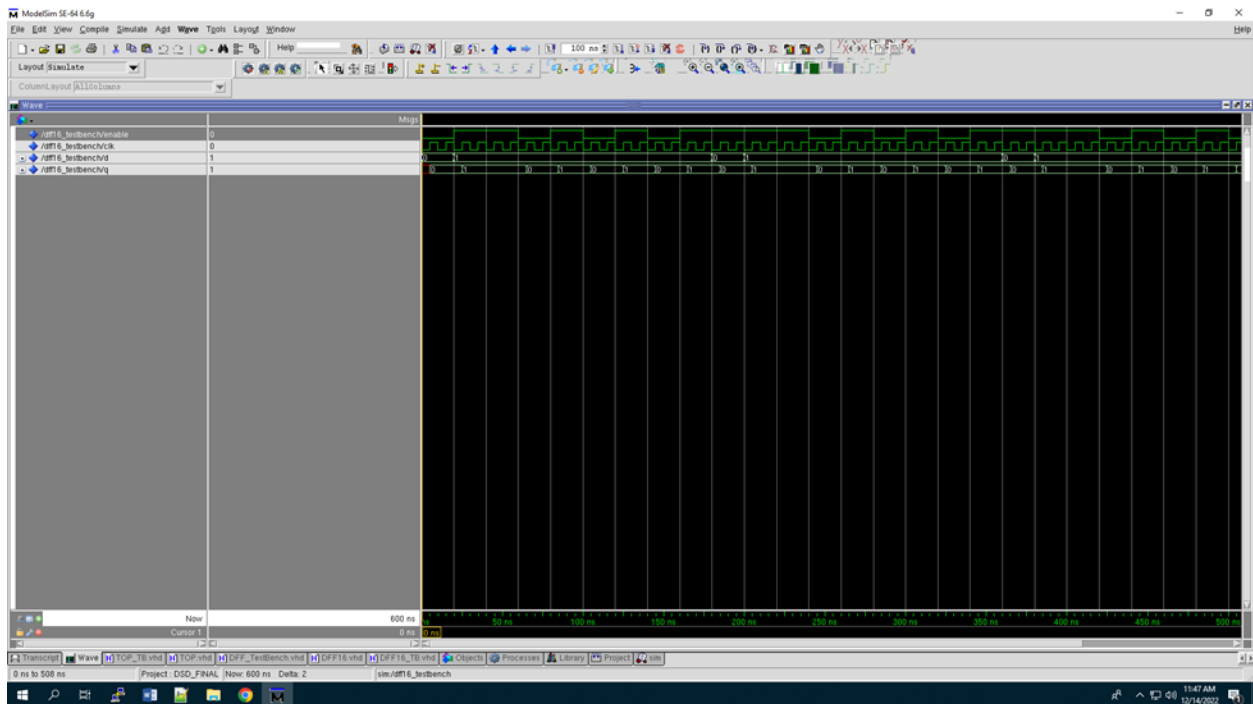


Figure 10: Simulation Result for DFF16

MUX

 


Figure 11: MUX Synthesis

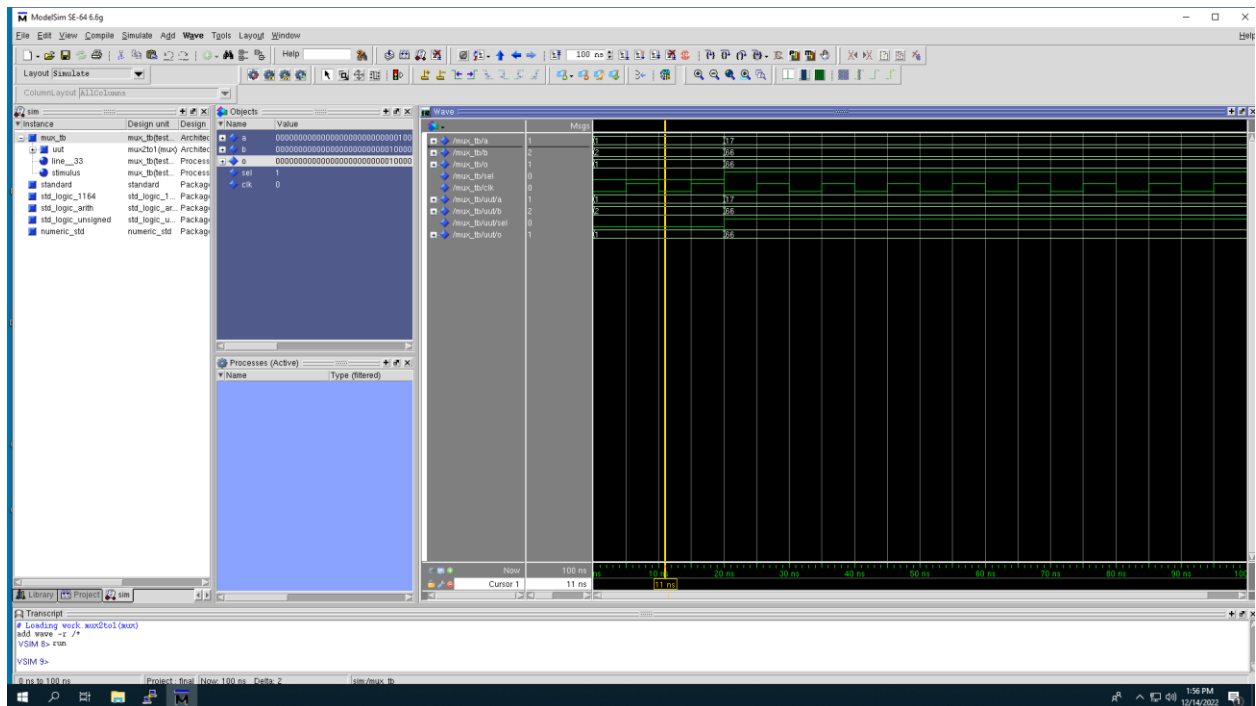


Figure 12: Simulation Result for MUX

FULL ADDER

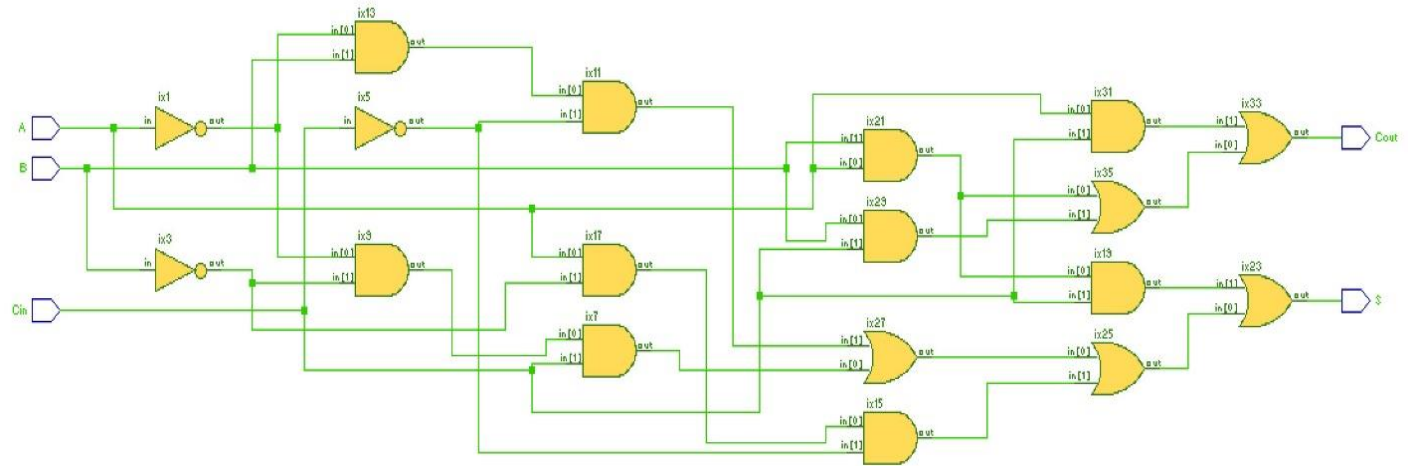


Figure 13: Full Adder Synthesis

 


Figure 14: Full Adder32 Synthesis

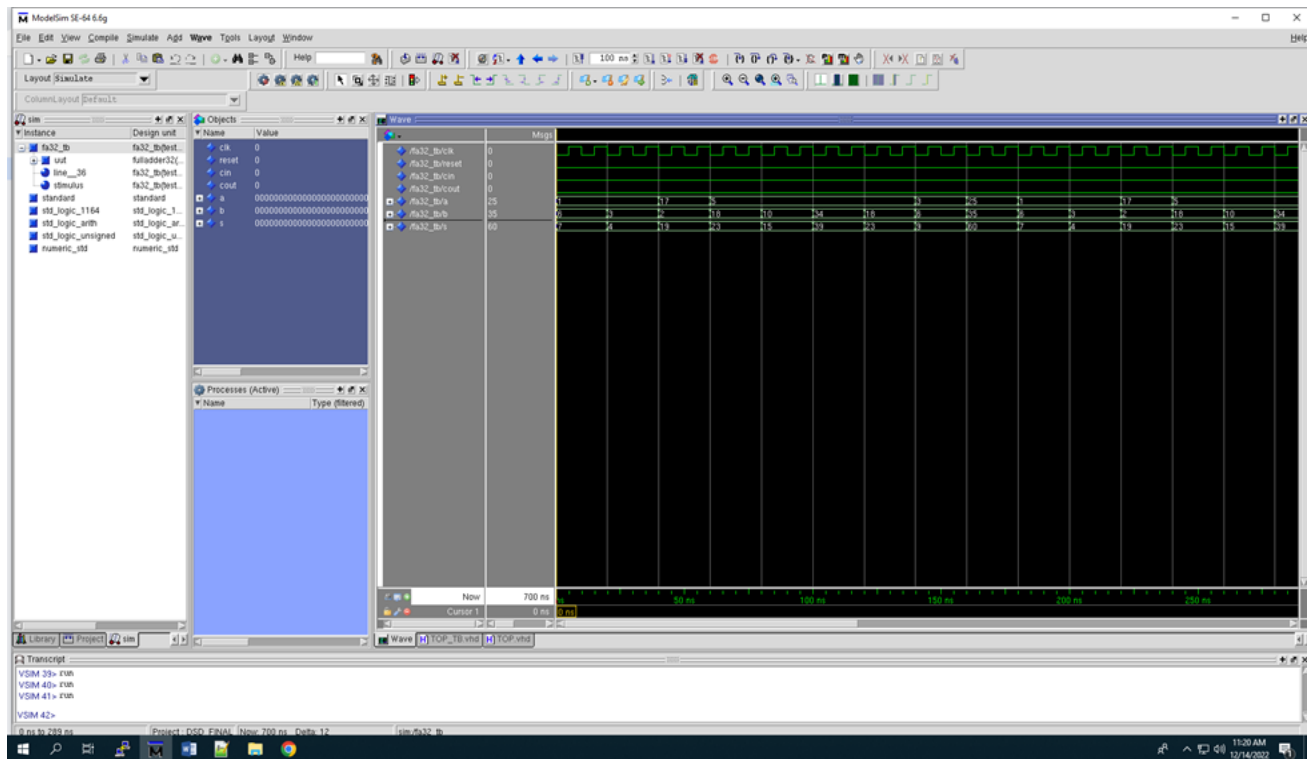


Figure 15: Simulation Result for Full Adder32

Multiplier

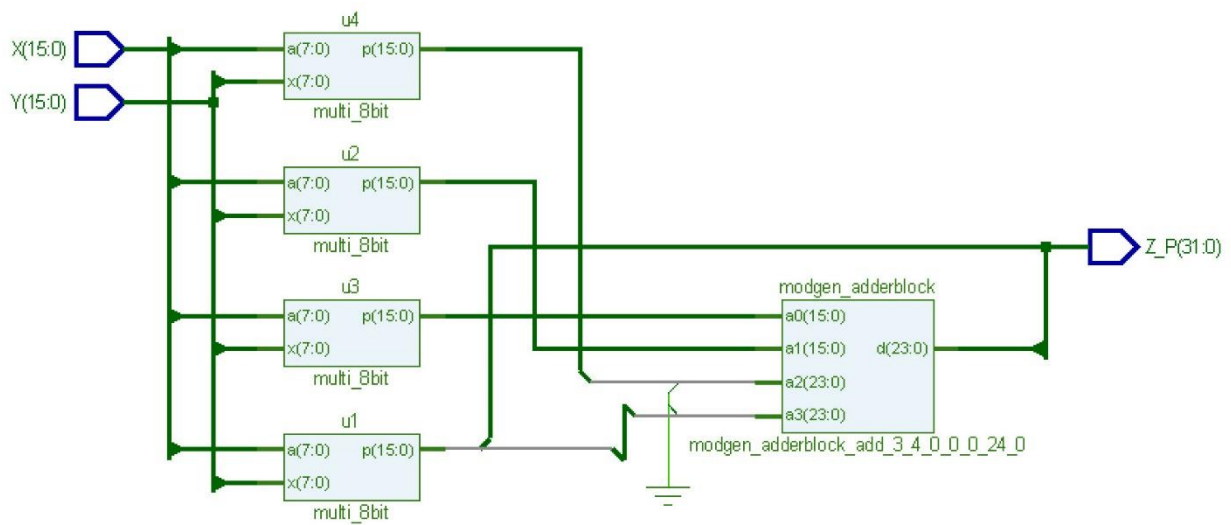


Figure 16: MULTIPLIER 16X16 Synthesis

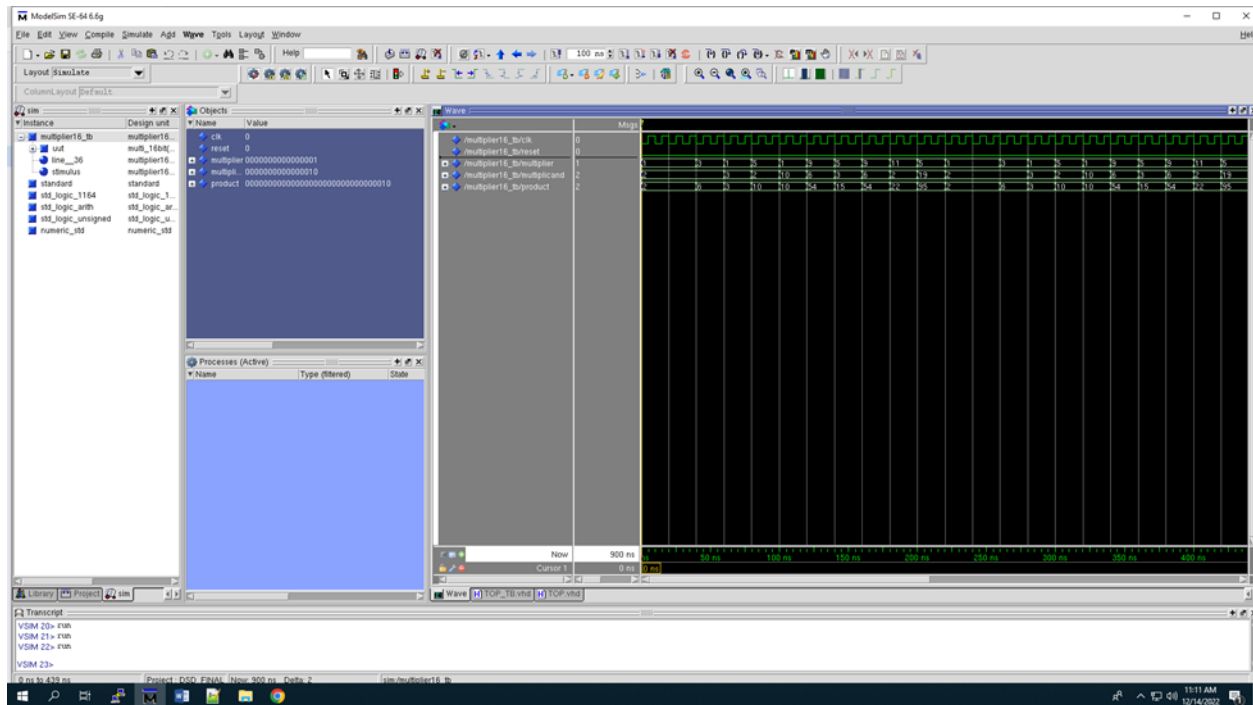


Figure 17: Simulation Result for MULTIPLIER 16X16

Multiplier Design

Design of an 8-bit Multiplier

The Multiplication algorithm used to multiply an 8-bit multiplier and an 8-bit multiplicand is as follows:

Consider we have to multiply the following two values: A(7 downto 0): A7, A6, A5, A4, A3, A2, A1, A0 and B(7 downto 0): B7, B6, B5, B4, B3, B2, B1, B0.

We make use of the AND gate to generate partial products (PP). Since we have an 8-bit multiplicand and multiplier, we will be generating, 8×8 , i.e., 64 Partial products.

 


Figure 19: 8-bit Array Multiplier Synthesis

The requirement for designing an 8-bit multiplier is as follows:

REQ1: 64 AND gates.

REQ2: 56 Full adders.

Design of a 16-bit multiplier using 8-bit multiplier

The Following is achieved by dividing the two 16-bit numbers, say m and n, into 8-bit numbers, I.e., mHigh, mLow and nHigh, nLow. The algorithm and the code are shown in the Figure below.

```

                                [mHigh mLow]    ×
                                [nHigh nLow]
                                - - - - -
                                [mHigh * nLow] [mLow * nLow]
                                [mHigh * nHigh] [mLow * nHigh]
                                - - - - -
                                [mHigh * nHigh] + [mLow * nHigh + mHigh * nLow] + [mLow * nLow]
                                - - - - -

-- 8x8 to 16x16

u1: multi_8bit PORT MAP ( mLow, nLow, mLow_nLow);
u2: multi_8bit PORT MAP ( mHigh, nLow, mHigh_nLow);
u3: multi_8bit PORT MAP ( mLow, nHigh, mLow_nHigh);
u4: multi_8bit PORT MAP ( mHigh, nHigh, mHigh_nHigh);

mHigh_nHigh_32(15 DOWNT0 0) <= mHigh_nHigh(15 DOWNT0 0);

first <= to_integer(unsigned(mLow_nLow));
second <= to_integer(unsigned(mHigh_nLow));
third <= to_integer(unsigned(mLow_nHigh));
fourth <= to_integer(unsigned(mHigh_nHigh_32));
|

sum <= fourth + (third + second)*256 + first;
Z_P <= STD_LOGIC_VECTOR(to_signed(sum, 32));

END MULTIPLIER_16;
```

Figure 20: Design of a 16-bit multiplier using 8-bit multiplier

Technical implementation

Implementation of CLEAR operation

When the clear flag is high, the inputs are multiplied by 0.

```
BEGIN
  A_IP <= ( 15 DOWNT0 0 => (NOT CLR)) AND A;
  B_IP <= ( 15 DOWNT0 0 => (NOT CLR)) AND B;
```

Implementation of LOAD operation

First, all the input flags are set. Then the inputs are loaded into the register when the load is high.

```
-- LOAD AT POS
LD_POS <= LOAD;
CLR_POS <= CLR;
LOAD_IN <= LD_POS;

-- LOAD INPUTS IN FLIP FLOP
FF0_A_IP : DFF16 PORT MAP ( d => A_IP, enable => LOAD_IN, clk => CLK, q => A_REG);
FF0_B_IP : DFF16 PORT MAP ( d => B_IP, enable => LOAD_IN, clk => CLK, q => B_REG);
```

Implementation of the END FLAG

The End flag is set and passed into a flip-flop as a control signal for the next stage.

```
-- END FLAG SETTING
END_FLAG <= CLK OR LD_POS;
--FF0_LD_EF: DFF PORT MAP (d => LD_POS, enable => FF0_LD_EN, clk => CLK, q => END_FLAG);
```

Implementation of the Arithmetic Unit

- STEP 1. The clear flag is set and pushed to the register
- STEP 2. 16-bit multiplication with output as PRODUCT_AB.

```
FF0_CLR_CF: DFF PORT MAP (d => CLR, enable => FF0_CLR_EN, clk => CLK, q => CLR_FLAG);

-- EQUATION STAGES 1/4[A x B]+1

-- A x B USING 16BIT MULTIPLIER

AB_MULT16 : multi_16bit PORT MAP (X => A_REG, Y => B_REG, Z_P => PRODUCT_AB);
```

- STEP 3. PRODUCT_AB is pushed into FF in stage 1 to propagate to the next stage.

STEP 4. Flags are passed to next stage

```
-- STEP 4 STAGE 1
S1_AxB_FF : DFF32 PORT MAP (d => PRODUCT_AB, enable => S0_EN_FF, clk => CLK, q => S1_AxB);
S1_E_FLAG : DFF PORT MAP (d => END_FLAG, enable => END_FLAG, clk => CLK, q => S1_END_FLAG);
S1_C_FLAG : DFF PORT MAP (d => CLR_FLAG, enable => CLR_FLAG, clk => CLK, q => S1_CLR_FLAG);

S1_EN_FF <= S1_END_FLAG;
```

STEP 5. The division operation is performed by concatenation with output as S2_SR_DIV_VAL, stage2.

STEP 6. S2_SR_DIV_VAL pushed into FF in stage 2 to propagate to the next stage.

STEP 7. Flags are passed to the next stage.

```
S2_SR_FF: DFF32 PORT MAP(d => S2_SR_DIV_VAL, enable => S1_EN_FF, clk => CLK, q => S2_SR_OP);
S2_E_FLAG : DFF PORT MAP (d => S1_END_FLAG, enable => S1_END_FLAG, clk => CLK, q => S2_END_FLAG);
S2_C_FLAG : DFF PORT MAP (d => S1_CLR_FLAG, enable => S1_CLR_FLAG, clk => CLK, q => S2_CLR_FLAG);

S2_EN_FF <= S2_END_FLAG;
```

STEP 8. Contains decimal '1' in the binary format of 32-bit.

STEP 9. The Addition operation of 1 and FF output from stage 2 is performed here:

```
-- STAGE 3 ADDITION
S3_ADD_OPERAND <= (0 => '1', OTHERS => '0');

S3_ADD_FA : FullAdder32 PORT MAP (A => S2_SR_OP, B => S3_ADD_OPERAND, Cin => '0', S => Z_OUT, Cout => FA_32_COUT);

MUX_OUT : MUX2TO1 PORT MAP (a => Z_OUT, b => (OTHERS => '0'), sel => S2_CLR_FLAG, 0 => Z_REG);

Z <= Z_REG;
```

TOP-Level Result

The figure below shows the final simulation result for the TOP level implementation.

 


Figure 21: Simulation Result of TOP-Level

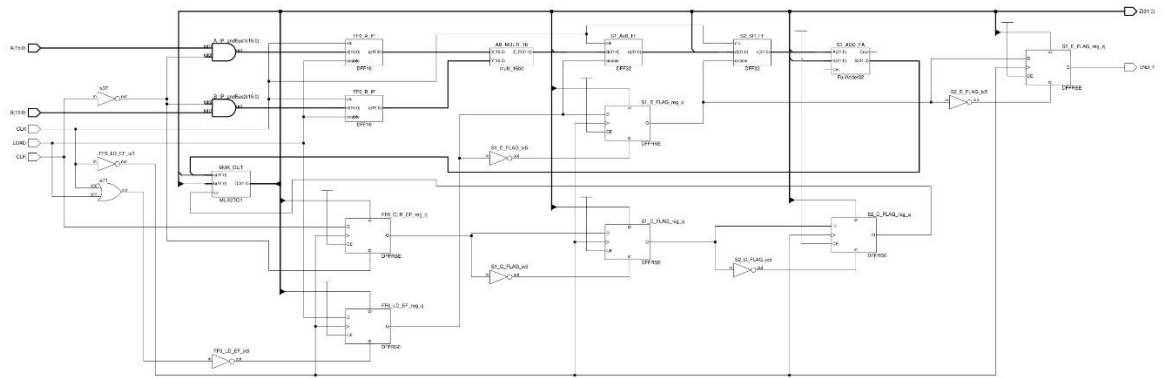


Figure 22: TOP-Level Synthesis

Precision RTL Area Report

```
// Precision RTL Synthesis 64-bit 2016.1.0.15 (Production Release) Wed Jun 8 09:35:56 PDT 2016
// Copyright (c) Mentor Graphics Corporation, 1996-2016, All Rights Reserved.
// Portions copyright 1991-2008 Compuware Corporation
// UNPUBLISHED, LICENSED SOFTWARE.
// CONFIDENTIAL AND PROPRIETARY INFORMATION WHICH IS THE
// PROPERTY OF MENTOR GRAPHICS CORPORATION OR ITS LICENSORS
// Running on Linux m_vah@poise.encs.concordia.ca #1 SMP Wed Nov 2 16:40:42 CDT 2022 3.10.0-1160.80.1.el7.x86_64 x86_64
// Start time Wed Dec 14 17:39:19 2022

*****
Device Utilization for 2VP100ff1696
*****
Resource          Used      Avail      Utilization
-----
IOs                68       1164       5.84%
Global Buffers     1         16       6.25%
LUTs              812      88192       0.92%
CLB Slices        406      44096       0.92%
Dffs or Latches    98       91684       0.11%
Block RAMs        0         444         0.00%
Block Multipliers  0         444         0.00%
Block Multiplier Dffs 0       15984       0.00%
GT_CUSTOM         0         20         0.00%
-----

*****

Library: work      Cell: TOP      View: TOP_LEVEL

*****

Cell              Library  References      Total Area

BUFGP             xcv2p    1 x
FDR_1             xcv2p   98 x           1 98 Dffs or Latches
FullAdder32       work     1 x           59 59 gates
                  49       49 LUTs

GND               xcv2p    3 x
IBUF              xcv2p   34 x
LUT1              xcv2p    6 x           1 6 LUTs
LUT2              xcv2p   62 x           1 62 LUTs
LUT3              xcv2p   40 x           1 40 LUTs
LUT4              xcv2p   24 x           1 24 LUTs
MUXCY_L           xcv2p   46 x           1 46 MUX CARRYs
OBUF              xcv2p   33 x
VCC               xcv2p    1 x
XORCY             xcv2p   48 x
multi_8bit        work     1 x          158 158 LUTs
                  183     183 gates
multi_8bit_unfolded0 work     1 x          159 159 LUTs
                  185     185 gates
multi_8bit_unfolded1 work     1 x          160 160 LUTs
                  185     185 gates
multi_8bit_unfolded2 work     1 x          160 160 LUTs
                  185     185 gates

Number of ports :           68
Number of nets :          519
Number of instances :        401
Number of references to this view : 0

Total accumulated area :
Number of Dffs or Latches :          98
Number of LUTs :          812
Number of MUX CARRYs :          46
Number of gates :          930
Number of accumulated instances :     1082
```

Figure 23: Device Utilization

Resources

1. GitHub: <https://github.com/abishekat/DSD>

Challenges

The red lines in the simulation output for the END_FLAG is due to flip-flops because the flip-flop functions at the clock event. The issue was later resolved.

Conclusion

We successfully implemented an Arithmetic unit to perform the operation $\mathbf{Z} = \frac{1}{4} [\mathbf{A} * \mathbf{B}] + \mathbf{1}$. The additional requirement of a 16-bit multiplier and multiplicand was also implemented. The pipelining of the system is done through flip-flops in three stages. The control path of the system is controlled using the following flags LD_POS, CLR_POS, LOAD_IN, FF0_LD_EN, FF0_CLR_EN, S0_EN_FF, S1_EN_FF and S2_EN_FF.

References

1. M. Mahapatro et al., "Design of Arithmetic Circuits Using Reversible Logic Gates and Power Dissipation Calculation," 2010 International Symposium on Electronic System Design, 2010, pp. 85-90, doi: 10.1109/ISED.2010.25.
2. Y. Duanmu, J. Yang, J. Li, X. Xue, M. Jing and X. Zeng, "A 16-bit Arithmetic Logic Unit Design by Using Gate Diffusion Input," *2020 IEEE 15th International Conference on Solid-State & Integrated Circuit Technology (ICSICT)*, 2020, pp. 1-3, doi: 10.1109/ICSICT49897.2020.9278245.
3. COEN-6521-2221-CC <https://moodle.concordia.ca/>. [Online]
4. <https://github.com/abishekat/DFT/blob/main/GROUP%2013%20REPORT.pdf>